

## AIM OF THE EXPERIMENT:- 7

To study the op-amp as an inverting amplifier and non-inverting amplifier

### EQUIPMENTS REQUIRED:-


- |                              |      |
|------------------------------|------|
| 1. Op-AMP trainer kit        |      |
| 2. Audio frequency generator | 1no  |
| 3. Decade resistance box     | 1nos |
| 4. CRO DSO                   | 1no  |
| 5. Digital multimeter        | 1no  |

### PROCEDURE:-

Apply sine wave 2V RMS from Audio signal generator at 1KHz frequency.  
Measure the output at different  $R_i$ .

#### CIRCUIT DIAGRAM

##### Inverting amplifier:

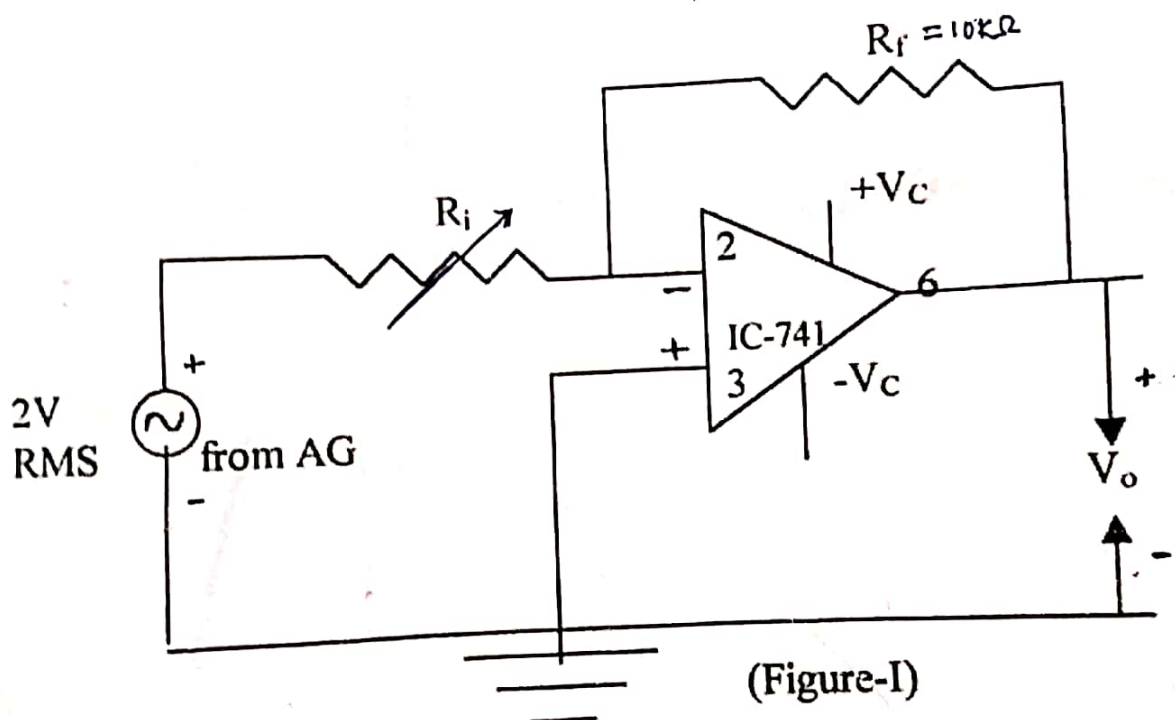


$$V_{out} = - (R_f/R_i) V_{in} \text{ for output AC 2V}$$

( $R_i=10\text{ K}\Omega$ ,  $5\text{ K}\Omega$  and  $2.5\text{ K}\Omega$ )

**TABLE-1**

$R_i$	$R_f$	$V_{in}$	$V_{out}$	Experimental gain = $V_o/V_i$	Theoretical gain	$\phi$

**Non – Inverting amplifier:**

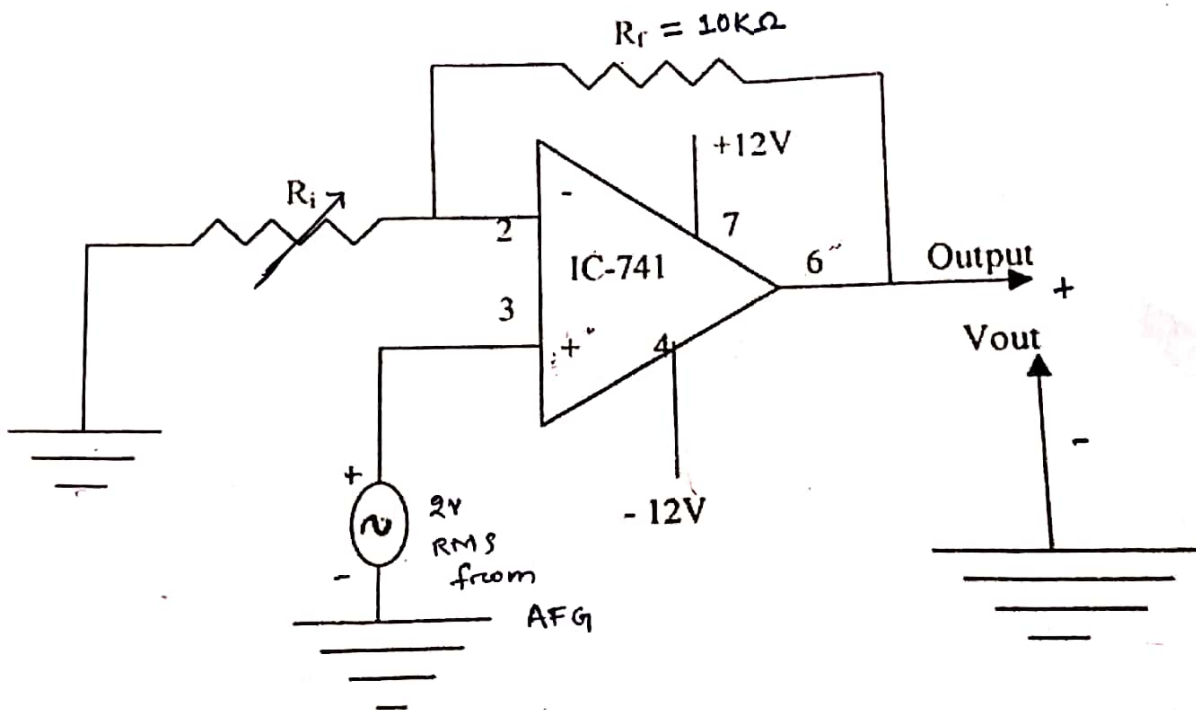

**TABLE-II**

$R_i$	$R_f$	$V_{in}$ in volt	$V_{out}$ in volt	Experimental gain = $V_o/V_i$	Theoretical gain	✓

$$V_o = (1 + R_f/R_i) V_{in}$$

Compare the experimental result with theoretical value and discuss

- \* WRITE THEORY (FROM BOOK) BEFORE PROCEDURE
- \* WRITE CONCLUSION (AT LAST).