

## **AIM OF THE EXPERIMENT (9)**

To observe, trace & measure the effect on the output waveforms of different clipper circuit.

## **EQUIPMENTS REQUIRED**


1. Transistor power supply (TPS)
2. Audio signal generator/Function generator
3. CRO

## **COMPONENTS REQUIRED**


1. Diode (IN4007)
2. Resistor (1K Ohm)
3. DC supply
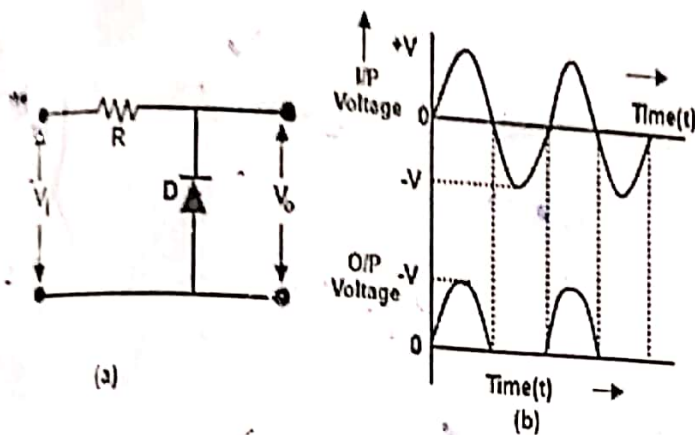
## **PROCEDURE**


Make connection as per the circuit diagram shown. Trace and measure the output voltage using CRO by applying  $10V_{p-p}$  sine wave from audio generator/FG as input.




Shunt (parallel) Negative Clipper

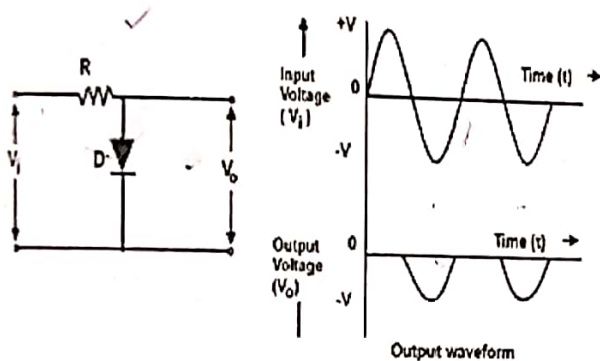


Shunt (parallel) positive clipper

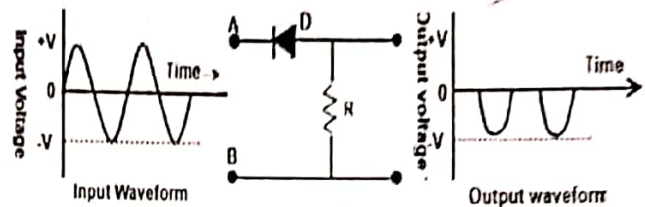


(a) Positive clipper

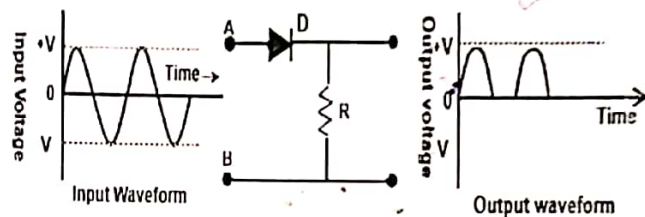

(b) Negative clipper

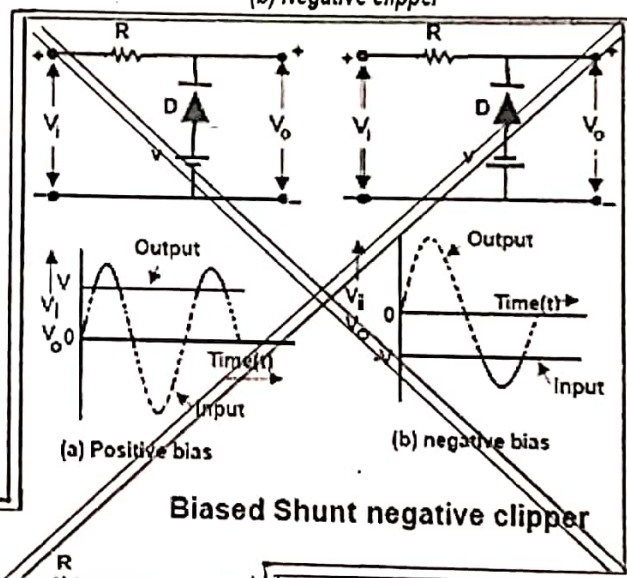

Biased Shunt negative clipper

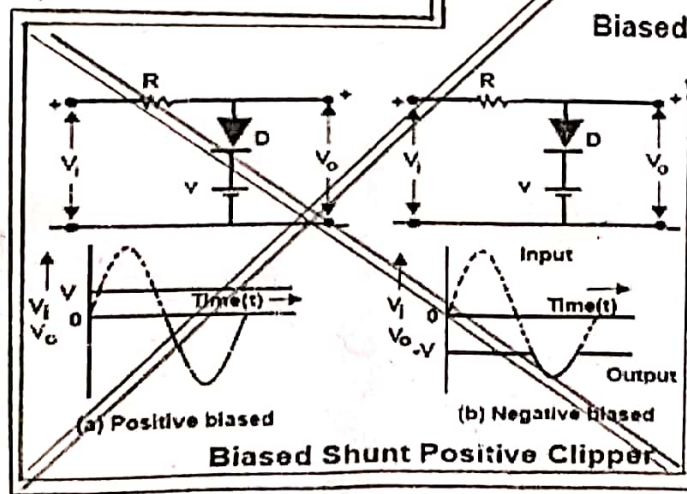

Biased Shunt Positive Clipper

## AIM OF THE EXPERIMENT

To observe, trace & measure the effect on the output waveforms of different clamper circuit.

## EQUIPMENTS REQUIRED

1. Transistor power supply(TPS)
2. Audio signal generator/Function generator
3. CRO

## COMPONENTS REQUIRED

1. Diode(IN4007)
2. Capacitor( $0.1 \mu\text{farad}$ )
3. Resistor( $100\text{K Ohm}$ )
4. DC supply

## PROCEDURE

Make connection as per the circuit diagram shown. Trace and measure the output voltage using CRO by applying  $10V_{p-p}$  sine wave from audio generator/FG as input

